

Bus Contention

Saturday, November 15, 2025 3:43 PM

- Since we have an open-drain output (pull line LOW or High-Z), many devices can be connected without causing damage during contention (multiple pulling LOW).

↳ Thus we get an AND output because if any device pulls low, the entire line goes low.

Push-Pull Scenario

- In this config, devices can actively drive HIGH (unlike the passive high in I2C) and actively pull low.
- If one device drives high and another drives low on the same line, our output is indeterminate. Also, push-pull devices typically use CMOS (remember NMOS and PMOS from Physics & EE), and those transistors have low resistances (R_{DS}) when in triode operation, so we're now dumping a huge amount of current during contention which can damage them.