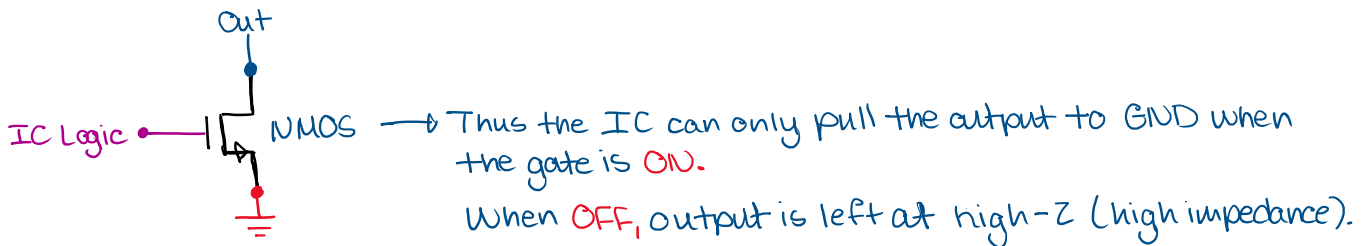


Connection

Thursday, November 13, 2025 9:35 PM

- **Open-drain connection:** Can only pull the line LOW or leave it in high-Z. Can NOT drive it high, you need a pullup resistor.



Remember for cut-off: $V_{GS} < V_T$

- Both SDA and SCL are **open-drain**, thus they need pull up resistors to have **HIGH** outputs. They both implement NMOS transistors.

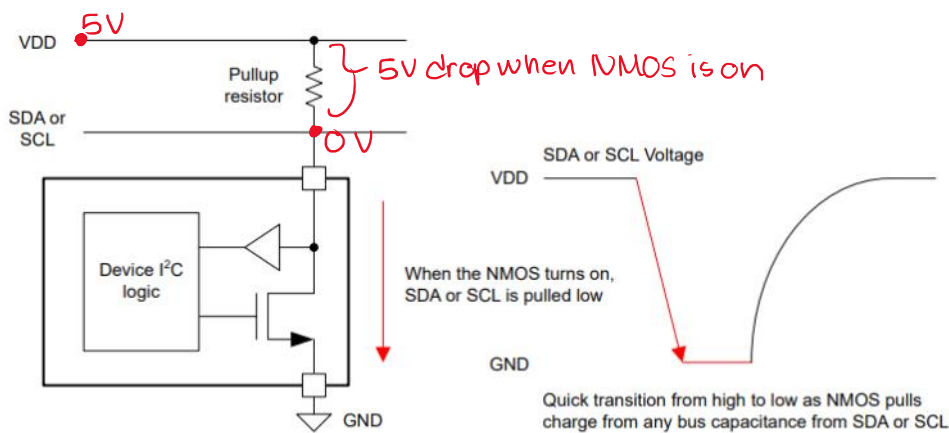


Figure 2-2. Open-Drain Connection Pulls Line Low When NMOS is Turned On

- When the NMOS is **ON**, current is pulled through the resistor to GND. Thus we have a 5V drop across the resistor which makes the output **LOW**.
- When the NMOS is **OFF**, it acts like an open circuit, so clock/data is left **HIGH**.
- TLDR, you can think of the NMOS as an active-low switch.